

California State University,  
Northridge

College of Engineering &  
Computer Science

Electrical and Computer  
Engineering Department

ECE 443L Digital Electronics  
Laboratory Report 9

CMOS Based ADC Circuit



By Haroutun Haroutunian

**Abstract:** After constructing the Analog-to-Digital Converter, students examine the Pulse Voltage supplies to alter input frequencies. Input frequencies alter the pulse, as seen in the output figures in Procedure.

**Keywords:** ADC, MSB, LSB, non-inverting

### 9.1 Introduction

Experiment 9 introduces students to Analog-to-Digital Circuits. ADCs are found in every electronic device, eg. Smartphones to convert volume on speakers, etc. The circuit consists of simple resistors, OpAmp, Voltage supplies to create inputs, and PMOS and NMOS transistors.

### 9.2 Simulation and Experimental Set-up

As seen in figure 9.1, the circuit is set up with common source and gate transistors. The circuit is set up where the Left-most is the Most Significant Bit, and the Right-most is the Least Significant Bit.

### 9.3 Simulation and Experimental Results

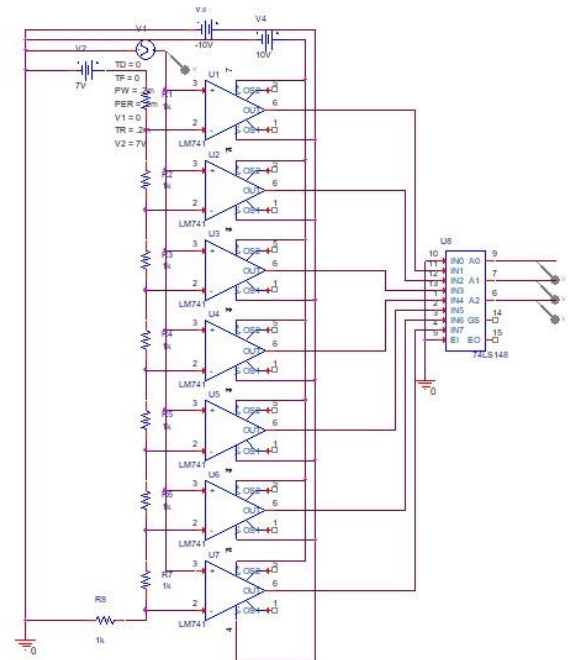


Figure 9.1 Case 2 7V Ramp Schematic with a freq @ 5kHz ADC Circuit

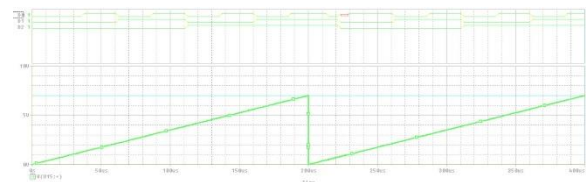


Figure 9.2 Case 2 Waveform 7V Ramp with a freq @ 5kHz ADC Circuit

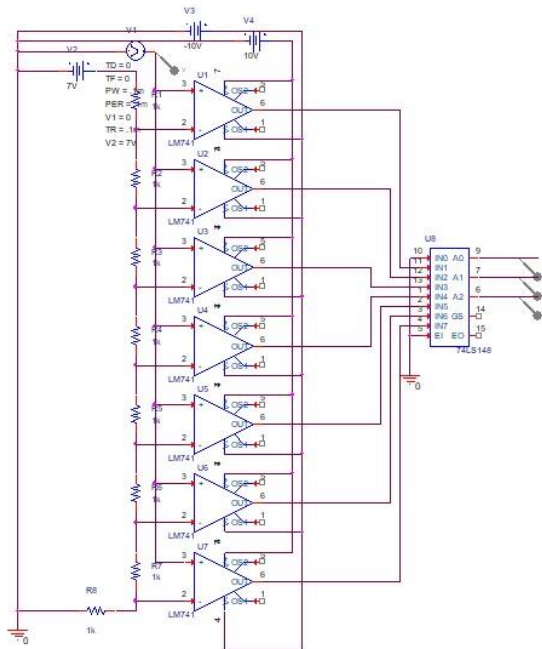


Figure 9.3 Case 4 7V Ramp  
Schematic with a freq @ 15kHz  
ADC Circuit

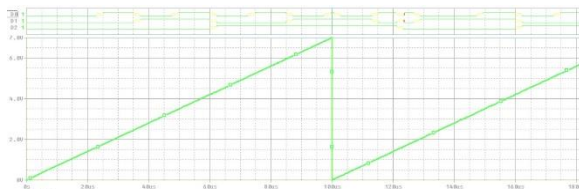


Figure 9.4 Case 4 Waveform 7V  
Ramp with a freq @ 5kHz ADC  
Circuit

## 9.4 Discussion and Conclusion

In experiment 8, students were exposed to the set-up and uses of ADC circuits. ADC is utilized in everyday electronic devices so real-world inputs can be read by the electronic device and output easy-to-read waveforms. The music industry is surrounded by ADC circuits since frequencies are input in analog or digital and converted.